



Phys 202

Recitation 3

Sunny Guha

<http://people.physics.tamu.edu/sunnyguha/teach.html>

Formulae

$$R = \frac{V}{I}.$$

Series :

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots.$$

Parallel:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots.$$

Kirchhoff's junction (or point) rule:


The algebraic sum of the currents into any junction is zero; that is,


$$\sum I = 0.$$

Kirchhoff's loop rule:


The algebraic sum of the potential differences in any loop, including those associated with emf's and those of resistive elements, **must equal zero**; that is,

$$\sum_{\text{around loop}} V = 0.$$

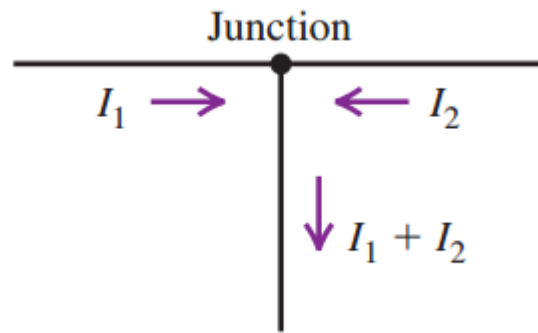

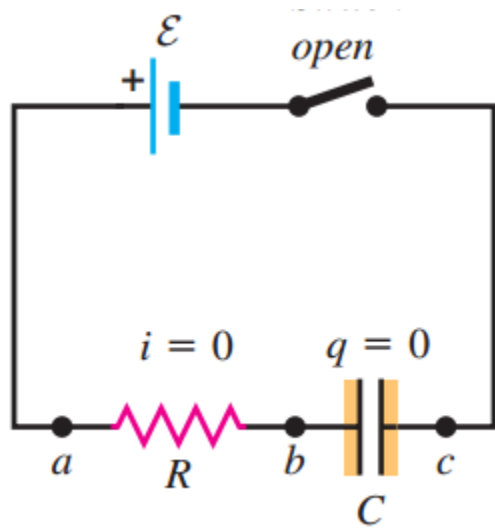


$$\mathcal{E} = iR + \frac{q}{C}.$$

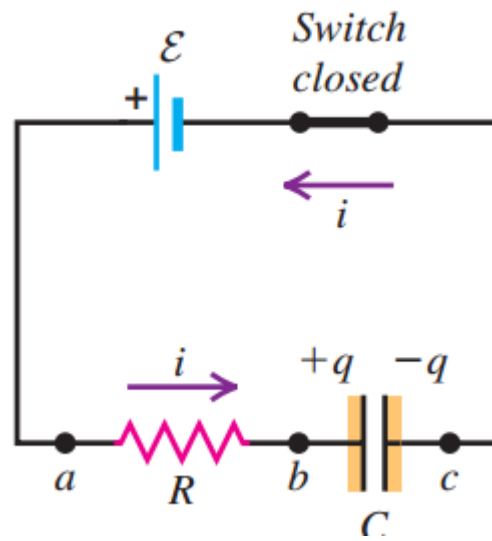


$$\mathcal{E} = \frac{q}{C} \quad \text{and} \quad q = Q_{\text{final}} = C\mathcal{E}.$$

$$i = I_0 e^{-t/RC}, \quad q = Q_{\text{final}} (1 - e^{-t/RC}).$$

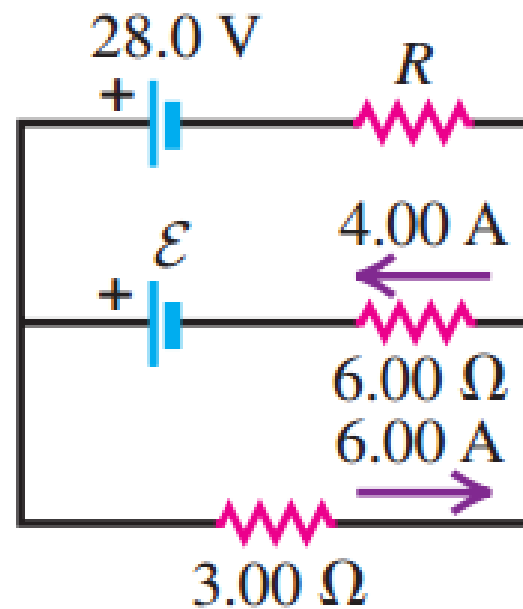●● In the circuit shown in Figure 19.60, find (a) the current in resistor R , (b) the value of the resistance R , and (c) the unknown emf \mathcal{E} .



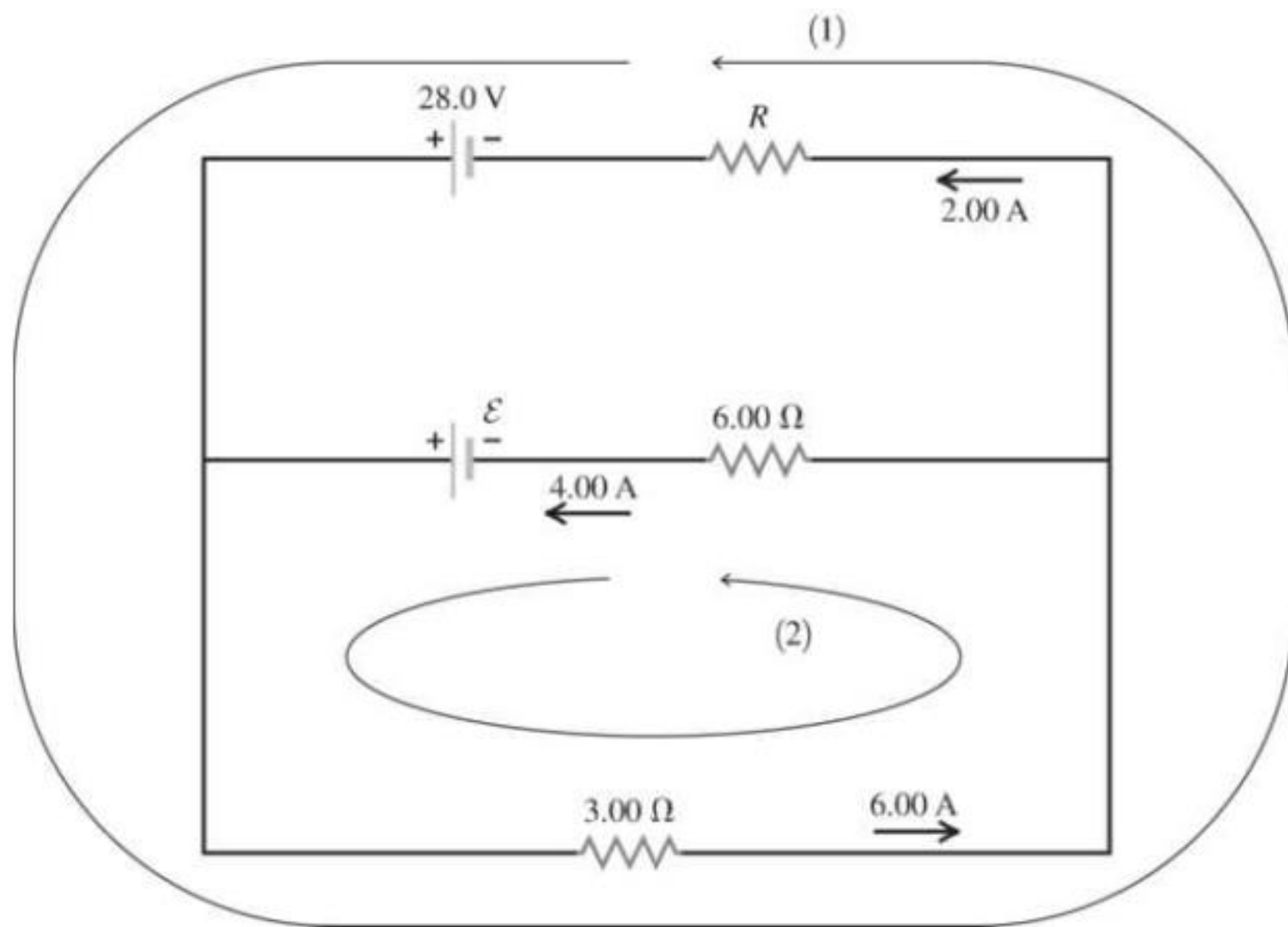

Solve: (a) The junction rule gives that the current in R is 2.00 A to the left.

(b) The loop rule applied to loop (1) gives:

$$-(2.00 \text{ A})R + 28.0 \text{ V} - (6.00 \text{ A})(3.00 \Omega) = 0.$$

$$R = \frac{28.0 \text{ V} - 18.0 \text{ V}}{2.00 \text{ A}} = 5.00 \Omega.$$

(c) The loop rule applied to loop (2) gives:

$$-(4.00 \text{ A})(6.00 \Omega) + \mathcal{E} - (6.00 \text{ A})(3.00 \Omega) = 0.$$

$$\mathcal{E} = 24.0 \text{ V} + 18.0 \text{ V} = 42.0 \text{ V}.$$

65. ●● A $12.4\ \mu\text{F}$ capacitor is connected through a $0.895\ \text{M}\Omega$ resistor to a constant potential difference of $60.0\ \text{V}$. (a) Compute the charge on the capacitor at the following times after the connections are made: 0 , $5.0\ \text{s}$, $10.0\ \text{s}$, $20.0\ \text{s}$, and $100.0\ \text{s}$. (b) Compute the charging currents at the same instants. (c) Graph the results of parts (a) and (b) for t between 0 and $20\ \text{s}$.

Solve: (a) At $t = 0$ s: $q = C\mathcal{E}(1 - e^{-t/RC}) = 0$.

$$\text{At } t = 5 \text{ s: } q = C\mathcal{E}(1 - e^{-t/RC}) = (12.4 \times 10^{-6} \text{ F})(60.0 \text{ V})(1 - e^{-(5.0 \text{ s})/(11.1 \text{ s})}) = 2.70 \times 10^{-4} \text{ C.}$$

$$\text{At } t = 10 \text{ s: } q = C\mathcal{E}(1 - e^{-t/RC}) = (12.4 \times 10^{-6} \text{ F})(60.0 \text{ V})(1 - e^{-(10.0 \text{ s})/(11.1 \text{ s})}) = 4.42 \times 10^{-4} \text{ C.}$$

$$\text{At } t = 20 \text{ s: } q = C\mathcal{E}(1 - e^{-t/RC}) = (12.4 \times 10^{-6} \text{ F})(60.0 \text{ V})(1 - e^{-(20.0 \text{ s})/(11.1 \text{ s})}) = 6.21 \times 10^{-4} \text{ C.}$$

$$\text{At } t = 100 \text{ s: } q = C\mathcal{E}(1 - e^{-t/RC}) = (12.4 \times 10^{-6} \text{ F})(60.0 \text{ V})(1 - e^{-(100 \text{ s})/(11.1 \text{ s})}) = 7.44 \times 10^{-4} \text{ C.}$$

(b) The current at time t is given by: $i = \frac{\mathcal{E}}{R} e^{-t/RC}$.


$$\text{At } t = 0 \text{ s: } i = \frac{60.0 \text{ V}}{8.95 \times 10^5 \Omega} e^{-0/11.1} = 6.70 \times 10^{-5} \text{ A.}$$

$$\text{At } t = 5 \text{ s: } i = \frac{60.0 \text{ V}}{8.95 \times 10^5 \Omega} e^{-5/11.1} = 4.27 \times 10^{-5} \text{ A.}$$


$$\text{At } t = 10 \text{ s: } i = \frac{60.0 \text{ V}}{8.95 \times 10^5 \Omega} e^{-10/11.1} = 2.72 \times 10^{-5} \text{ A.}$$

$$\text{At } t = 20 \text{ s: } i = \frac{60.0 \text{ V}}{8.95 \times 10^5 \Omega} e^{-20/11.1} = 1.11 \times 10^{-5} \text{ A.}$$
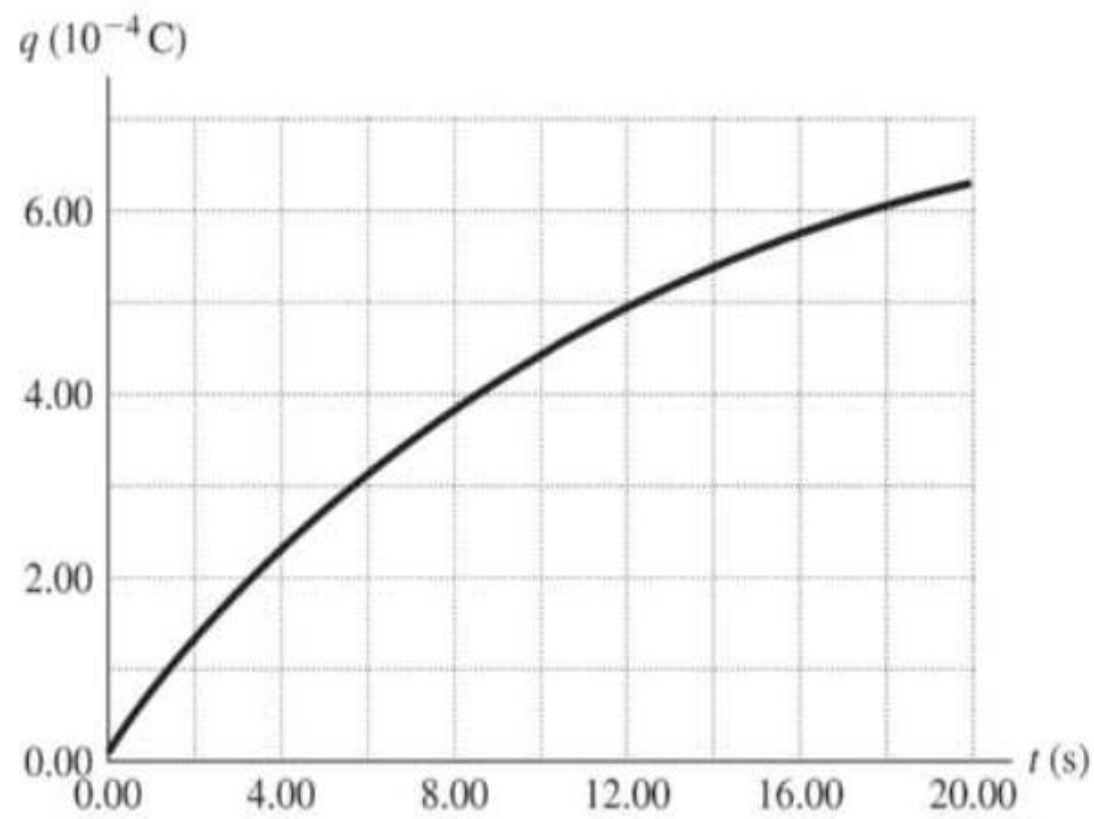
$$\text{At } t = 100 \text{ s: } i = \frac{60.0 \text{ V}}{8.95 \times 10^5 \Omega} e^{-100/11.1} = 8.20 \times 10^{-9} \text{ A.}$$



(a)

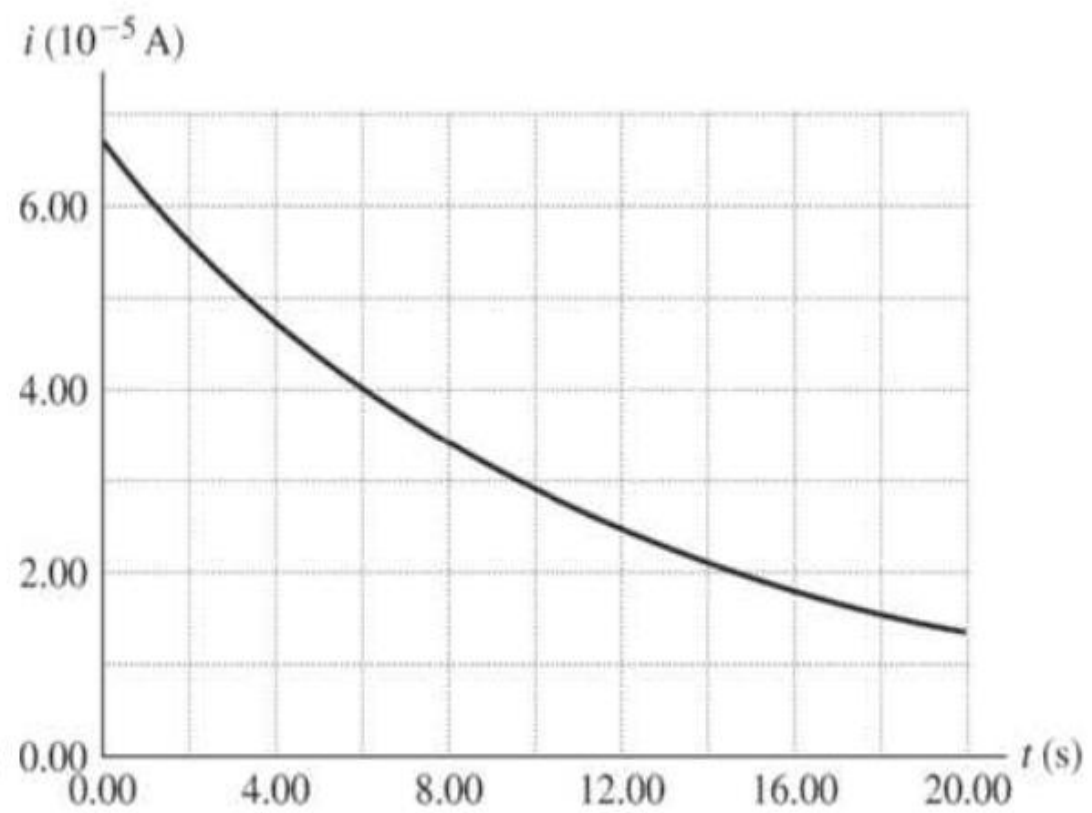

(b)

(5 pts) 11. Two resistors are connected to a 24 V battery as shown in the sketch. $R_1 = 3.0 \, \Omega$ and $R_2 = 6.0 \, \Omega$. What is the voltage across R_1 ?

